

Auto Correct

Static Voltage Stabilizer Using Igbt And Dsp



Utopia Automation & Control Pvt. Ltd.

P-4/5, Information Technology Park, Old MIDC, Satara, Maharashtra, INDIA

Contact us : 02162-246821, 246829

www.utopiacontrol.com

CONTENTS

Page

1.	Introduction	3
2.	Working	4
3.	Block diagram	6
4.	Waveforms	7
5.	Features	10
6.	Reliability	11
7.	Efficiency	12
8.	Comparison chart between static stabilizer and Conventional type stabilizers	14
9.	Technical specification	16


Utopia's Static Voltage Stabilizer is an IGBT based PWM type buck-boost voltage stabilizer which has tight regulation and fast correction speed which is impossible to obtain using conventional methods such as servo voltage stabilizers, SCR / triac type stabilizer, relay type stabilizer etc.

This is an SMPS type voltage stabilizer for mains voltage (AC input and AC output). This is a new switching topology where PWM is made directly in AC-to-AC switching, without any harmonic distortion. In this topology there is no need to convert the AC input to DC and again convert it back to regulated AC output. This simplifies the design, reduces the component count and improves the efficiency and reliability. The power stage is an IGBT chopper control. The chopping frequency is around 20KHz which ensures absolutely silent operation and pure sine wave output (no waveform distortion).

The control section is based on dsPIC controller which ensures quick correction of output which is not possible in conventional relay type stabilizer or servo controlled stabilizers. The circuit is having LCD for display which will show all parameters like: input voltage, output voltage, connected load, your company name (We will program your company name in the dsPIC at the time of technology transfer) etc.

Since the circuit is fully solid state (no mechanical or moving parts) there will not be any wear and tear like the brush tear in servo stabilizer or relay degrading in relay based stabilizer.

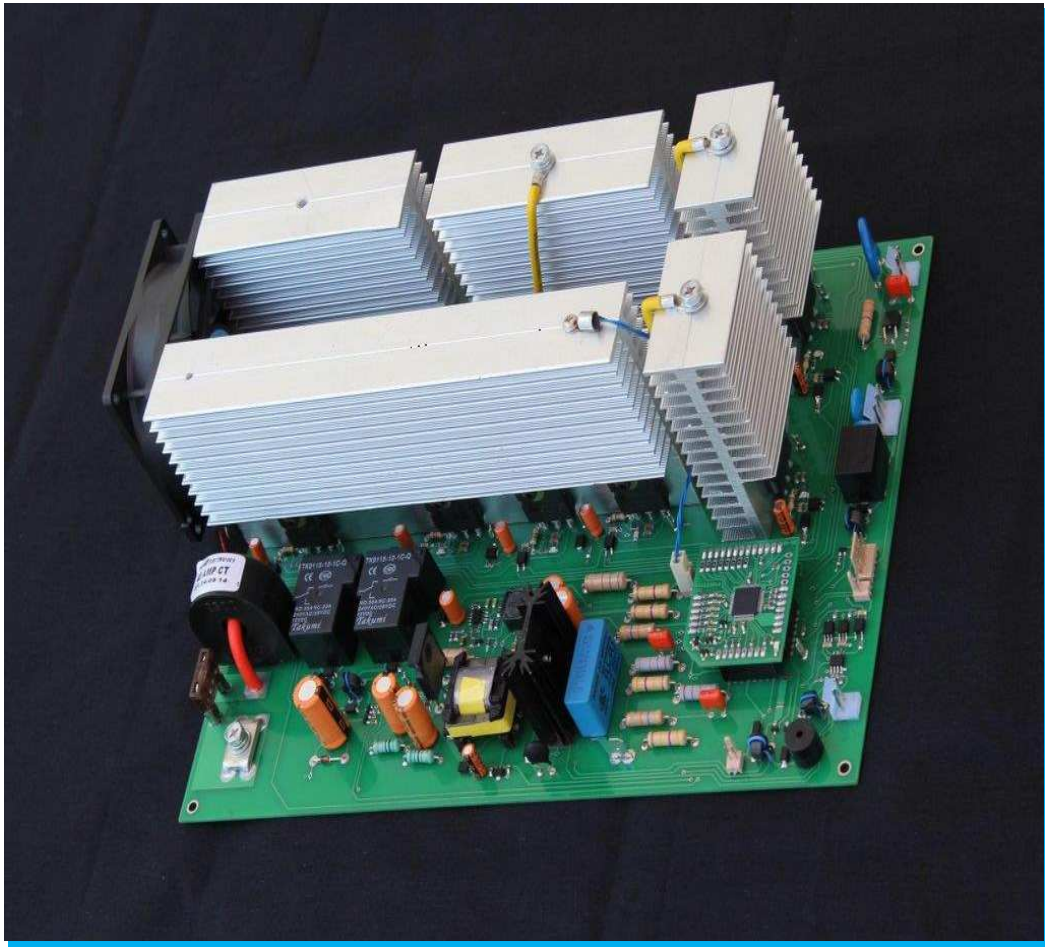This is specially useful in places where we need very fast correction speed, constant output voltage, overload current limiting and short circuit protection, soft start, high voltage cut-off and low voltage cut-off, automatic bypass, no wear and tear, long life and maintenance free which is impossible with other conventional relay type or servo control stabilizers.



Let me explain what it is in brief – In this IGBT based PWM type static voltage stabilizer only the difference voltage is switched through IGBT and will be added or subtracted from the mains. This is done electronically without any step changing in voltage which occurs when the system regulates. This is achieved by a feedback control system using digital signal processor (DSP). The output voltage is sensed by the DSP and corrections are made by varying the duty cycle of the PWM.

This stabilizer boosts up the voltage if it is low and bucks the voltage if it is high.

For example - If the AC input is 200V and the AC output is set for 220V, only 20V will be regulated through the IGBT and will be added to the original mains source which is 200V. If the AC input is 195V, then 25V will be added....

So the power and current in the IGBT will be very less (less than 1/5th of the total load if the range is 180V to 260V).

For example - In a 5KVA (5000VA) stabilizer if AC input is 195V, then 25V will go through the PWM stage.

So, the output current is $5000 / 220 = 22.7\text{A}$.


So, the difference power is $22.7\text{A} * 25\text{V} = 568\text{VA}$

Therefore, the current through the IGBT = $568\text{VA} / 195\text{V} = 2.9\text{A}$ only.

Similarly, if the AC input is 240V, then 20V will be subtracted.

This means, we can use discrete IGBTs and make the circuit very compact and very high efficient and cost effective. The efficiency in worst case will also be above 97%. This stabilizer is ideal for mobile towers, CNC machines, medical equipment, textile industries, power plants and any industrial product that needs tight regulation and fast correction. We can also use this for Air Conditioners, refrigerators, motor, pump etc.

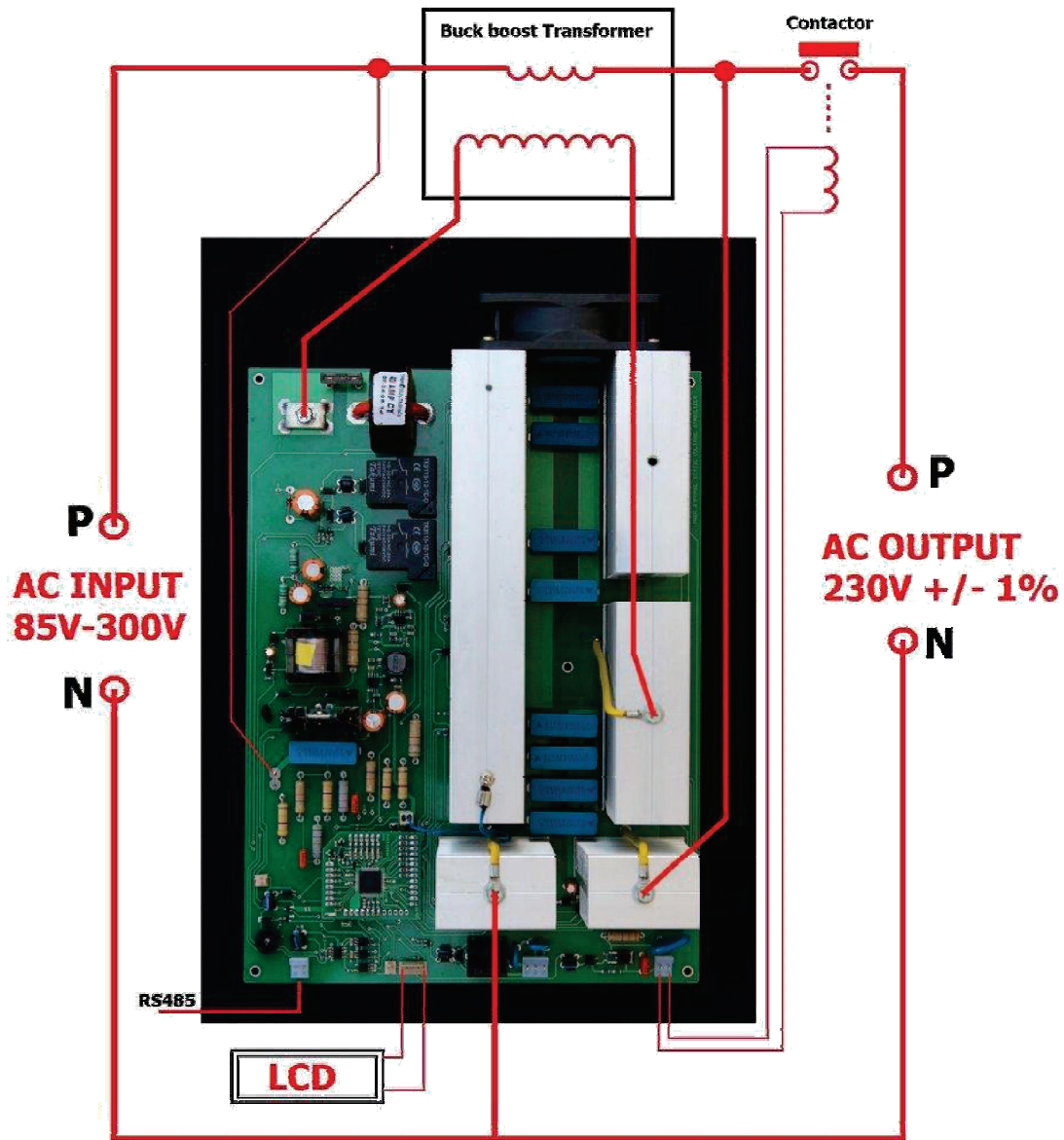The transformer size will be only $1/5^{\text{th}}$ of the output power. For 10KVA stabilizer transformer size will be that of 2KVA.




Highlights of Auto Correct are -

- Instantaneous correction speed - over 20000V per second
- Discrete IGBT up to 30KVA single phase and 90KVA three phase
- Single PCB for control stage, IGBT driver section and power stage.
- Lower BOM and easy to assemble.
- Single contactor for three phase system.
- Single LCD for three phases.
- All protections included - low voltage, high voltage, overload and short circuit.


The unique feature of this stabilizer is its correction speed which is very fast. If there is any change in the input voltage, it will be corrected in the very next cycle.

Channel 1 (yellow) is the input waveform.


Channel 2 (blue) is the output waveform.

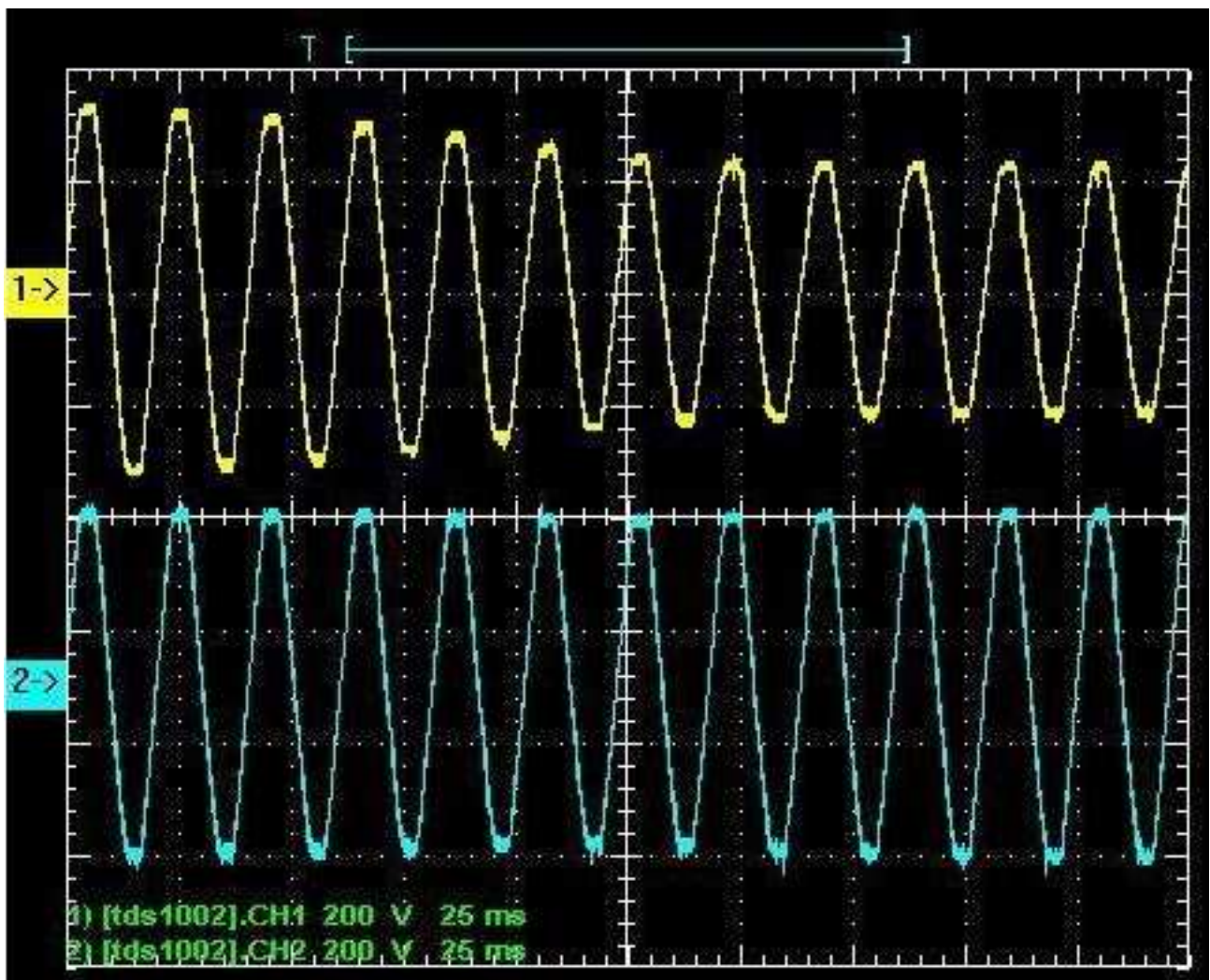

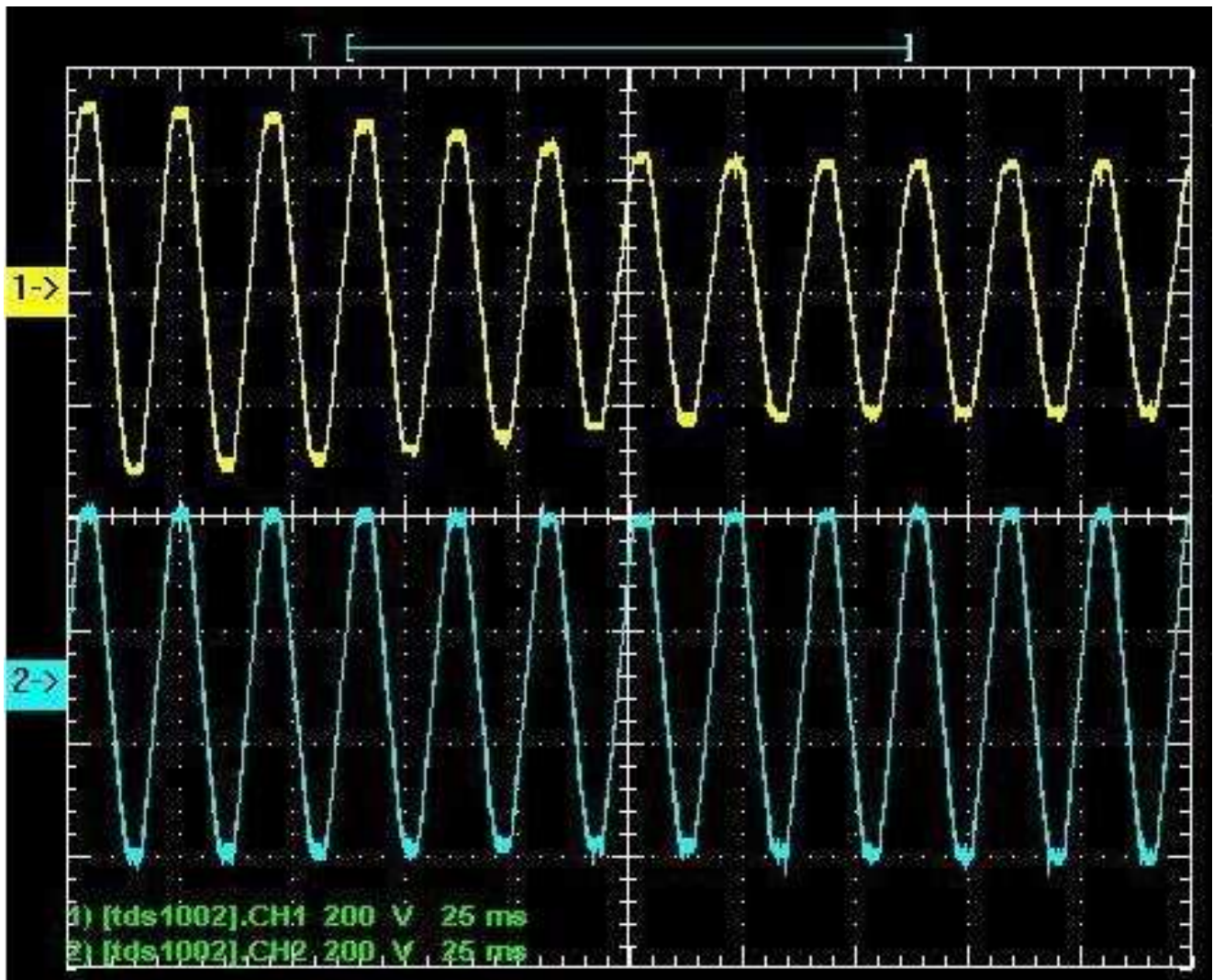As we can see in the above waveform, input voltage (channel 1 – yellow) is dragged down from high voltage to low voltage within 0.2sec, but the output voltage (channel 2 – blue) remains steady.



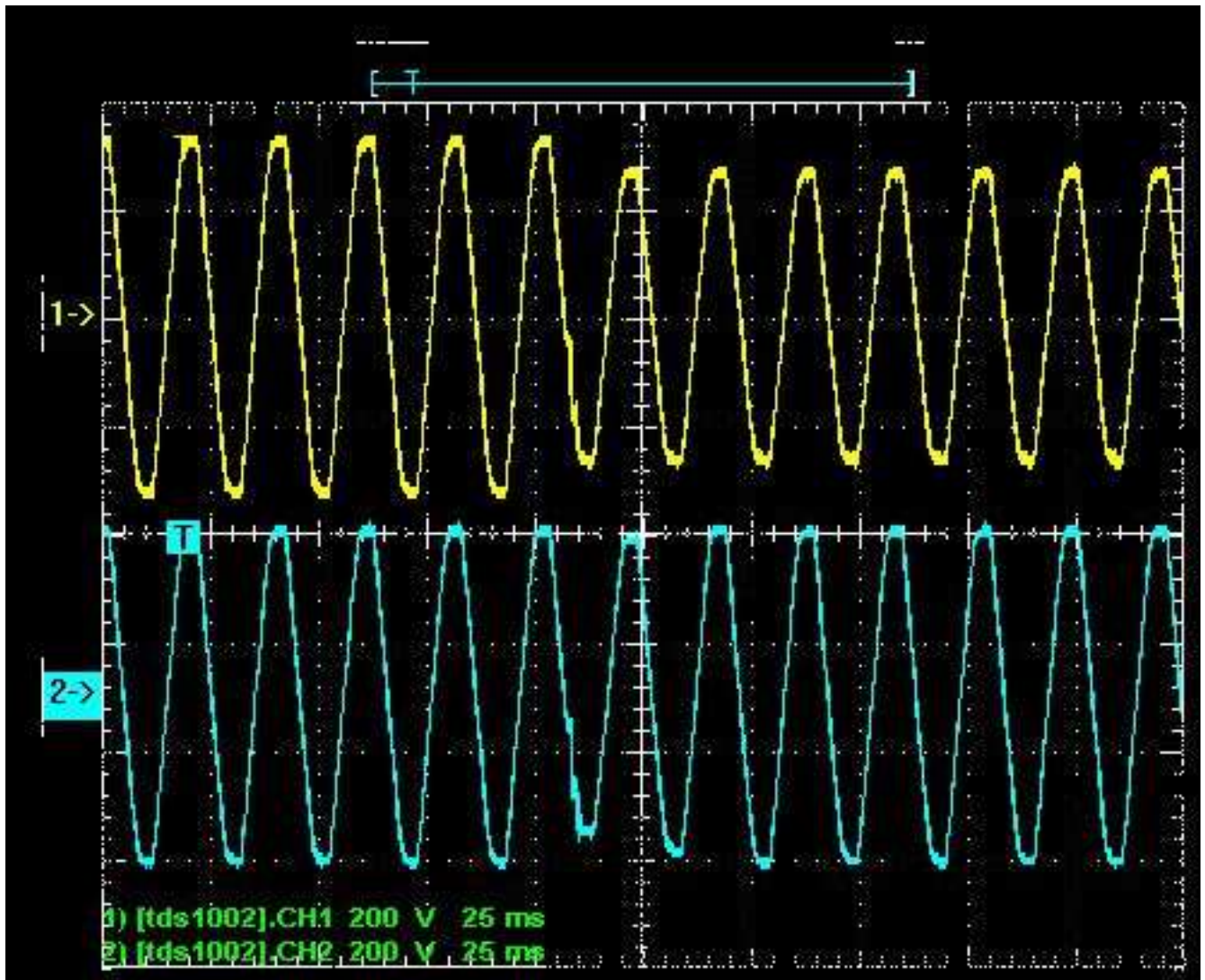Input voltage (channel 1 – yellow) is dragged up from low voltage to high voltage within 0.2sec, but the output voltage (channel 2 - blue) remains steady.



The input voltage (channel 1 – yellow) stepped down from high voltage to low voltage in no time, and the output voltage (channel 2 - blue) corrected immediately in the next cycle.

1. Direct AC-AC conversion without rectifying to DC improves the efficiency, reliability and reduces the components.
2. Rapid cycle by cycle correction of output. It can correct sudden fluctuation in the line voltage. For example using a welding machine in the same line will cause sudden fluctuation in the line voltage which can not be corrected with conventional relay type and servo controlled voltage stabilizers, where Static Voltage Stabilizer can correct it.
3. Output regulation of +/- 1% which is impossible in conventional stabilizer.
4. No distortion in output waveform.
5. Overload cutoff and short circuit cut off
6. Over voltage and under voltage cutoff.
7. Automatic bypass incase of failure.
8. LCD display for displaying all parameters and your company name.
9. Small transformer size ($1/5^{\text{th}}$ of the capacity)
10. Compact size and light weight
11. 20KHz PWM control
12. IGBT power stage. Highly reliable.
13. Fully solid state. No moving part, hence more life and no maintenance.
14. Silent operation.

1. Over load and short circuit protection: It has overload/ short circuit current limiting and cut-off, the control part of the static stabilizer will sense the output current and if the load is more than the rated VA, for example: In a 3KVA stabilizer, if you accidentally connect a load of 10KVA, it will limit the output current to the maximum output current at full load of the stabilizer.
2. High input voltage cut off : The high input voltage cut-off is set for 270V (it can be set for some other voltage also) up to 270V input, the output will be constant 220V. Because of this high voltage cut-off, the stabilizer itself will be protected from high voltage and the connected load is also safe.
3. Low voltage cut off : The low voltage cut off can be set at any value. For example – in a 180V to 260V model, the low voltage cut-off can be set at 180V or 170V or lower. Because of this low voltage cut off, the stabilizer is protected from low voltage malfunctioning.
4. Wear and tear : There is no wear and tear like the conventional stabilizer, as this stabilizer is fully solid state and there is no moving part. Because of this, there is no need of replacement of components even after certain period due to ageing. This eventually increases the reliability of the static stabilizer.

All the above protections and safety measures are not incorporated in the conventional stabilizers and that is what makes our differential power mode static stabilizer very reliable and unique.

It is because of the topology, this stabilizer has very high efficiency. In this topology, only the difference power is switched through the IGBTs as explained under the Working, $1/5^{\text{th}}$ of the total power is only switched through the IGBT even at the worst case. Otherwise it is less than $1/5^{\text{th}}$ of the total power in normal case.

So for a 10KVA stabilizer, in the worst case 2KVA is switched through the IGBTs. The current through the IGBT will be $2000\text{VA} \div 180\text{V} = 11\text{A}$.

- Conduction loss

The Infineon IGBT IKW75N60T has a voltage drop ($V_{ce(sat)}$) of 1.8V in worst case. So the conduction loss = $1.8\text{V} \times 11\text{A} = 20\text{VA}$. This will come in two IGBTs so the total conduction loss will be 40VA.

- Diode loss

The maximum diode forward voltage drop of the IGBT is 1.7V. So, the conduction loss in the diode is $1.7\text{V} \times 11\text{A} = 19\text{VA}$. This will come in two IGBTs so the total diode conduction loss will be 38VA.

- Switching loss

The optimum switching frequency selected is 18KHz so we can minimize the switching loss and there will not be any audible noise. The switching loss per IGBT at full load (11A) is measured to be 30VA. This will come in two IGBTs so the total switching loss will be 60VA.

- Transformer loss

The cost effective buck – boost transformer as per our winding data will have an efficiency above 95% at full load. So the loss in the transformer is 5%. Loss in the transformer = $2000\text{VA} \times 5\% = 100\text{VA}$.

The overall loss in the system = conduction loss + diode loss + switching loss + transformer loss

Which is, System loss = 40VA + 38VA + 60VA + 100VA = 238VA

Therefore, for an output of 10KVA (10,000VA), the input will be 10000VA + 238VA = 10238VA

So, the system efficiency = $\frac{\text{output power}}{\text{Input power}} \times 100 = \frac{10000}{10238} \times 100 = 97.68\%$

The overall system efficiency = 97.68%


We can easily achieve the buck-boost transformer efficiency of 98% using CRGO core, then the transformer loss will be 40VA at full load. So the overall system efficiency will be 98.25%.

Type of stabilizer	Advantages	Disadvantages
Servo voltage stabilizer	<ul style="list-style-type: none"> > Low technical skill > Less number of components > Easy to manufacture > High efficiency 	<ul style="list-style-type: none"> > Wear and tear due to the mechanical movement, requires periodic replacement of brushes. > Due to low correction speed there will be voltage overshoot and voltage dip > Heavy and bulky > No inrush current limiting for surge loads
Relay type voltage stabilizer	<ul style="list-style-type: none"> > Simple design > Easy to manufacture > Low cost > High efficiency 	<ul style="list-style-type: none"> > Periodic maintenance due to relay failure > Poor regulation > Interrupts load current during step change > Unsuitable for higher KVA operation > No inrush current limiting for surge loads

Type of stabilizer	Advantages	Disadvantages
SCR / triac type tap changing voltage stabilizer	<ul style="list-style-type: none"> > No moving part, less maintenance > Fast correction speed > High efficiency 	<ul style="list-style-type: none"> > Complex wiring > Stepped regulation so output is not tight regulated > Interrupts load current during step change > Not cost effective > No inrush current limiting for surge loads
Auto Correct IGBT PWM static voltage stabilizer	<ul style="list-style-type: none"> > No moving part, less maintenance > Tight regulated output +/-1% > Fast correction speed –over 20000V per second > Low cost > High efficiency > It has inrush current limiting for surge loads > Highly reliable 	<ul style="list-style-type: none"> > Not cost effective in lower KVA(below 2KVA)

Varying input given to servo stabilizer and Auto Correct

15

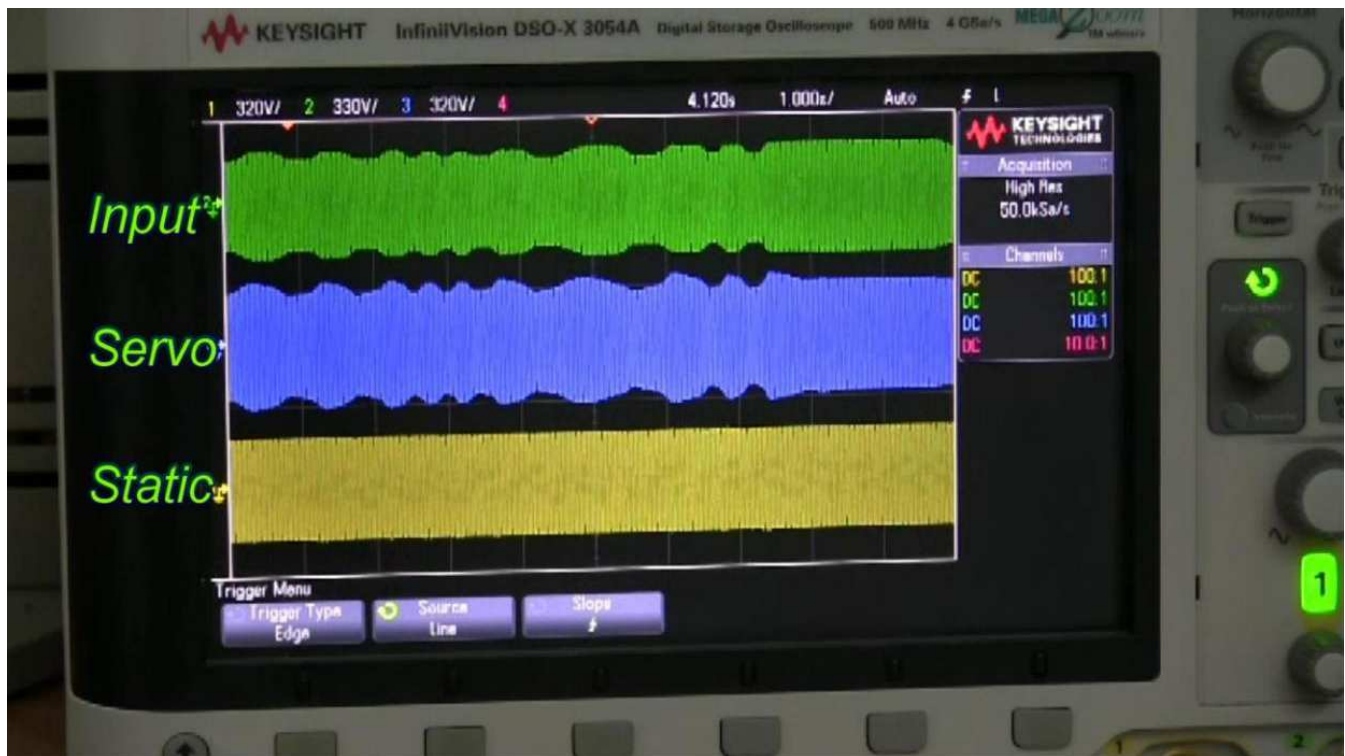

Particulars	Single Phase	Three Phase
Capacities Discreet IGBT based IGBT module based	1KVA to 30KVA 30KVA to 70KVA	3KVA to 90KVA 90KVA to 200KVA
Control type	DSP based IGBT PWM switching	DSP based IGBT PWM switching
Input Voltage Range for 220V output - Normal Wide Extended Input Voltage Range for 110V output - Normal Wide Extended	180V to 260V 150V to 290V 90V to 300V 90V to 130V 75V to 145V 45V to 175V	312V to 450V 260V to 500V 155V to 520V 155V to 225V 130V to 250V 78V to 300V
Output Voltage	220V +/- 1% settable 110V +/- 1% settable	380V +/- 1% settable 190V +/- 1% settable
Regulation	+/- 1%	+/- 1%
Efficiency	> 97%	> 97%
Input Frequency	45Hz to 65Hz	45Hz to 65Hz
Wave Form	Same as Input	Same as Input
Effect of power factor	nil	nil
Display	LCD for -Input voltage Output voltage Load VA Line frequency Overload High voltage input Low voltage input Cut off mode Bypass mode Set up mode Name of your company	LCD for -Input voltage Output voltage Load VA Line frequency Overload High voltage input Low voltage input Cut off mode Bypass mode Set up mode Name of your company
Rate of Correction	20000V per second	20000V per second
Operating Temperature	0 to 50 deg Celsius	0 to 50 deg Celsius
Duty cycle	Continuous	Continuous

Particulars	Single Phase	Three Phase
Nature of Cooling	Air Cooled	Air Cooled
Mains bypass	Auto bypass to mains when stabilizer is on cut off mode and mains input voltage is between 190V to 250V.	Auto bypass to mains when stabilizer is on cut off mode and mains input voltage is between 190V to 250V.
Protections	Overload Short circuit High voltage Low voltage	Overload Short circuit High voltage Low voltage
Trip & Restart	Auto	Auto
Transformer	1/5 th size of the rated VA	1/5 th size of the rated VA

